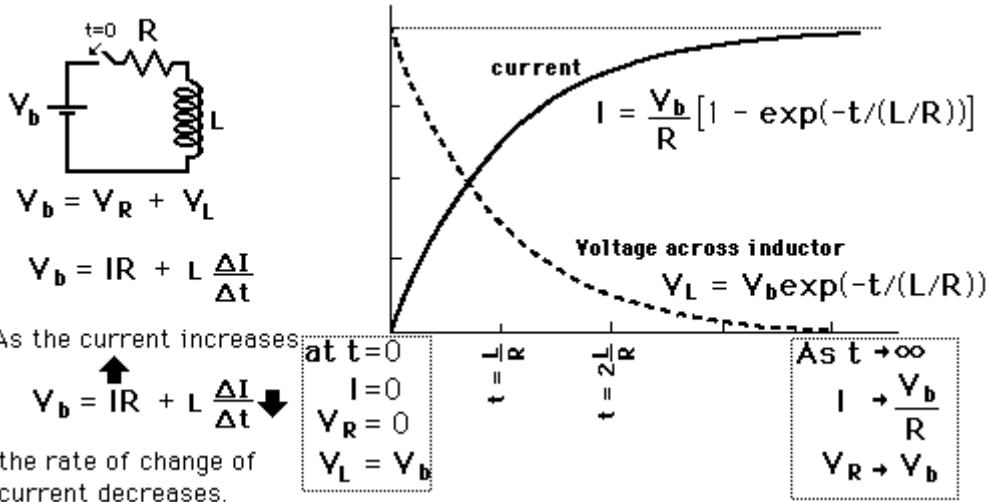


Inductor Transient

When a battery is connected to a series [resistor](#) and [inductor](#), the inductor resists the change in current and the current therefore builds up slowly. Acting in accordance with [Faraday's law](#) and [Lenz's law](#), the amount of [impedance](#) to the buildup of current is proportional to the rate of change of the current. That is, the faster you try to make it change, the more it resists. The current builds up toward the value it would have with the resistor alone because once the current is no longer changing, the inductor offers no impedance. The rate of this buildup is often characterized by the [time constant](#) L/R . Establishing a current in an inductor stores [energy in the magnetic field](#) formed by the coils of the inductor.



[Calculation](#)

[Index](#)


[DC Circuits](#)

[Inductor Concepts](#)

[HyperPhysics***** Electricity and Magnetism](#)

[Go Back](#)


Inductor Transient Calculation

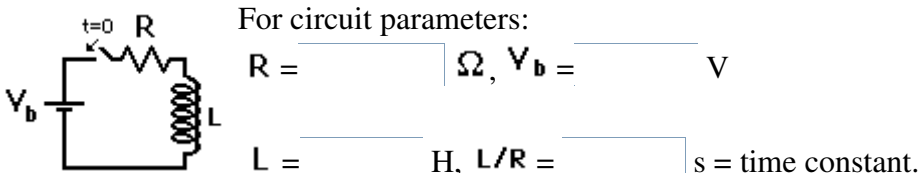

[Index](#)

[DC Circuits](#)

[Inductor Concepts](#)

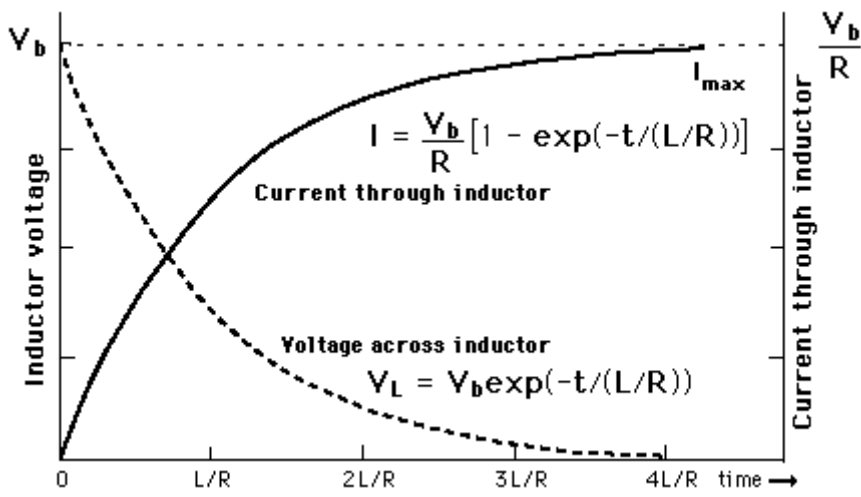

This circuit will asymptotically approach a maximum current of $I_{max} = \frac{V_b}{R} =$ A

since the inductor voltage approaches zero.

At time $t =$ s = L/R

The charging current is = $I_{max} =$ A

and the inductor voltage is = $V_b =$ V

[Inductor transient discussion](#)

[HyperPhysics](#)***** [Electricity and Magnetism](#)

[Go Back](#)